

Active Bandpass Filter

Dual Opamp Based Active Bandpass Filter

Ali Raheem*

3rd of April 2021

Contents

Introduction

A dual opamp based active bandpass filter, I'm using the LM358. The board uses one half of the LM358 to create a virtual ground and then the other one to amplify between a low pass and high pass RC network. It's laid out like this to simplify as much as possible design of each stage. The two 100K resistors could be of any equal value, ideally large for power efficiency.

I think I might re-jig the board to use a cascade filter on both sides for sharper cut offs as when using it for a narrow band you end up with reduced gain at the centre frequency.

The last version was made by OSHPark. The cost was \$9.10 for 3 boards.

Pin Compatible opamps

I think the layout is pretty standard.

- LM358
- NE5532
- TLC27M7

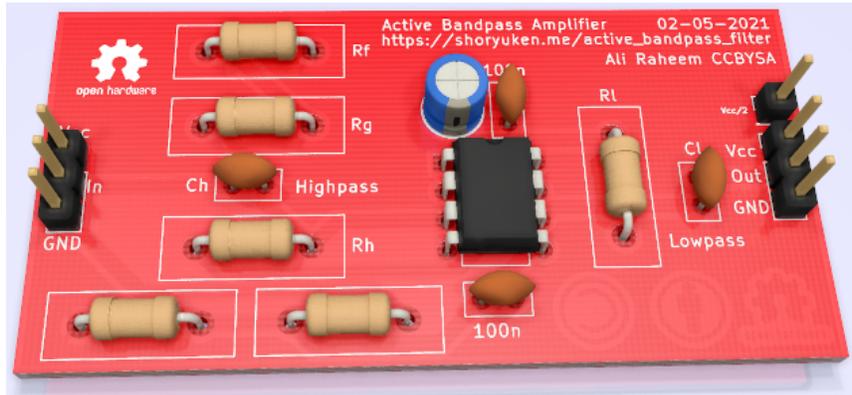


Figure 1: KiCad render of the PCB.

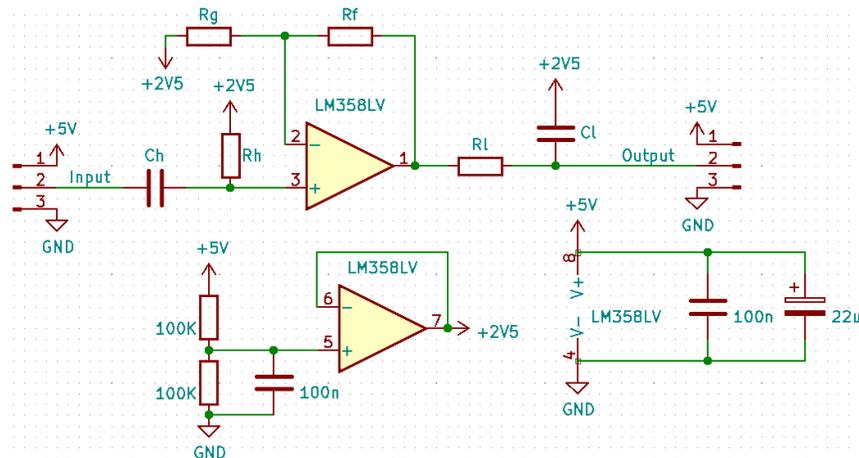


Figure 2: First the high pass filter decouples input, then it's amplified as controlled by R_F/R_G . A virtual ground is also created with the two 100K resistors.

Schematic

A full PDF for the schematic is attached below.

Between the RC filter networks is a non-inverting opamp amplifier with gain, $A_v = 1 + \frac{R_F}{R_G}$. The RC filters have a -3dB frequency at $\frac{1}{2\pi RC}$.

PCB

The KiCad and Gerber files are attached below, the layout is simple. The power planes are fairly random with a small capacitive effect for the V_{CC} and $\frac{V_{CC}}{2}$ supplies.

Professionally Made

I ordered a set from OSHPark, as always the purple and gold combo is absolutely banging.

Manufacturer	OSHPark	JLCPCB
Layers	2	2
Width	45.3mm	45.3mm
Height	26.0mm	26.0mm
Boards	3	5
Cost	\$9.10	\$9

OSHPark is a little more expensive (you get 5 boards from JLCPCB for the price of 3 from OSHPark), and the boards from OSHPark come with these nasty sprues that you have to file off (see in figure 3).

That said I am very happy with the quality. I'll likely order a set of boards from JLCPCB with a few changes, mainly using full-sized resistor footprints (1/4 W) and braking out $V_{CC}/2$.

Example Usage

I've used it for a few small purposes, it was easy to solder even with the small resistor spacing. The new version will use full-sized resistor spacing.

*blog@shoryuken.me

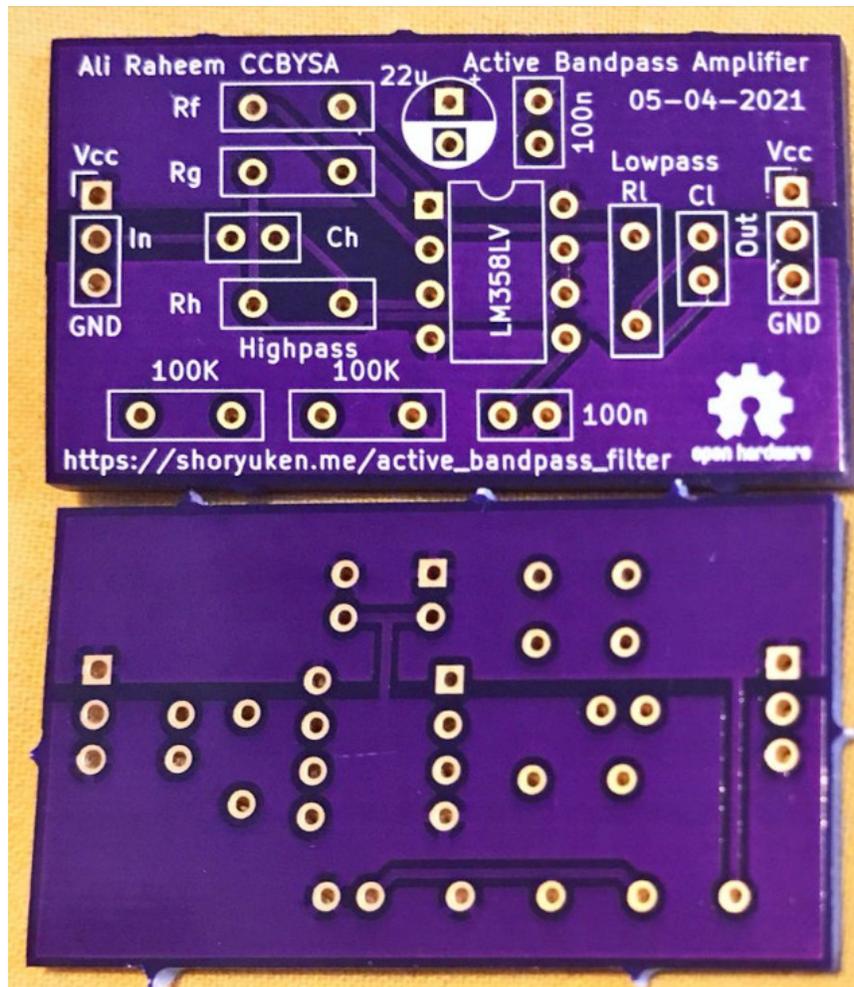


Figure 3: And a small but simple layout PCB for through-hole parts. The boards came with jagged sprue remnants (below) I filed off (above).

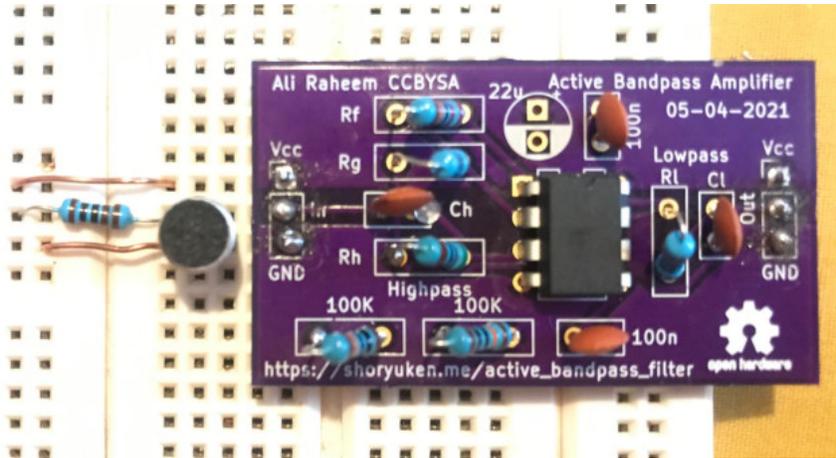


Figure 4: An electret microphone amplifier with a pass of 350-700Hz, output is clean around $0.2V_{PP}$. Soldering was... poorly done.

Files

- KiCad and Gerber Files
- Schematic PDF
- Home Etch PDF

Changes

02-05-2021 Breakout $\frac{V_{CC}}{2}$

01-05-2021 Included OSHPark examples

08-04-2021 Widen tracks, why so thin???

05-04-2021 Switch back to dual OPAMP with single supply. Ordered from OSHPARK.

04-04-2021 Switch to quad opamp with virtual ground.

03-04-2021 High pass first to act as coupling stage.

Other Formats

- Web
- Text
- PDF